
Nama: Reza Aristo Rifandi


Kelas : D


NIM : L200180206

1. Carilah datasheet IC 7442! Cari schematic yang menunjukkan gerbang logika penyusun IC 7442!


- Datasheet IC 7442

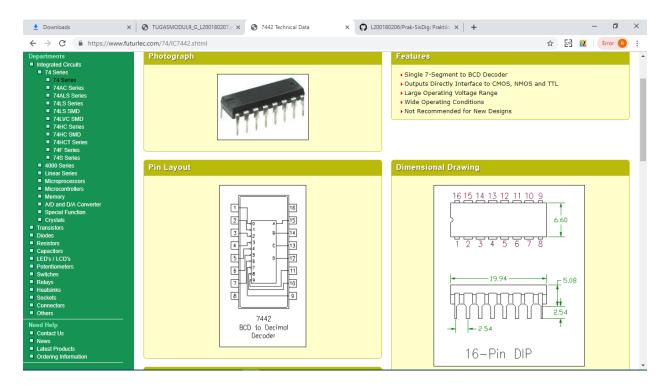

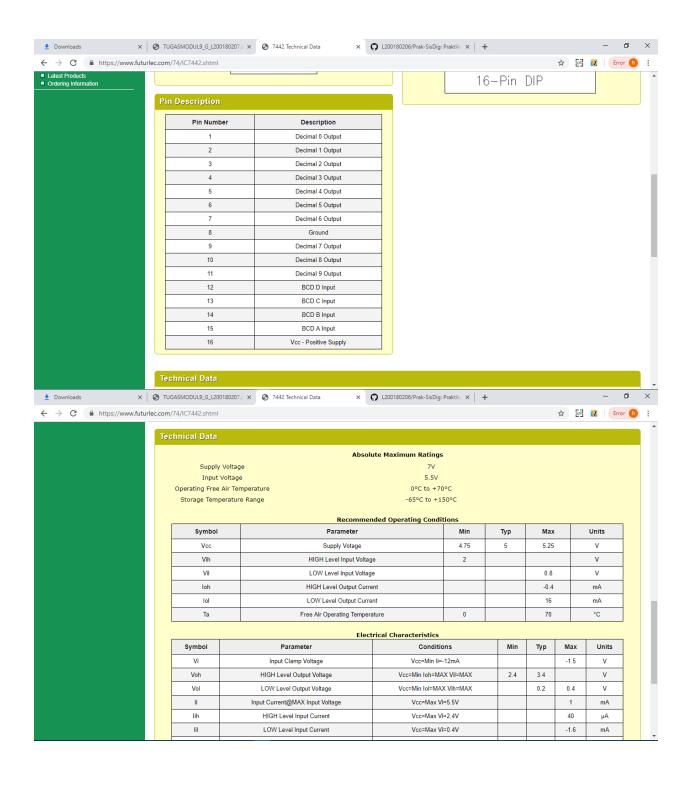

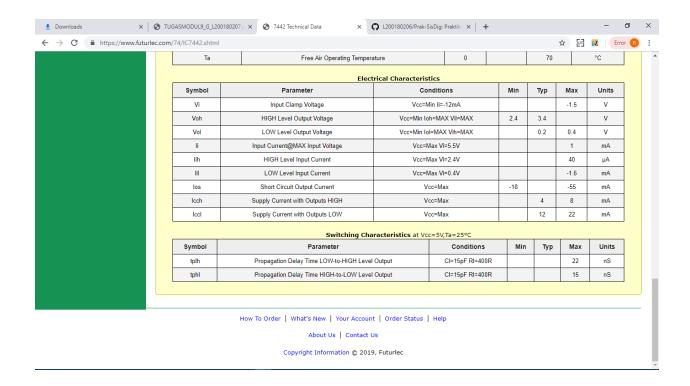

- Schematic IC 7442

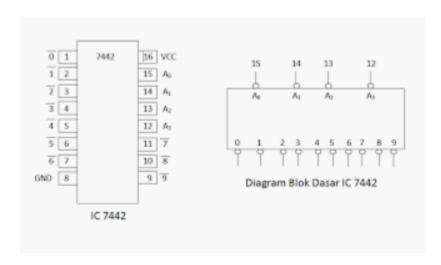

output Q0 1	fopa	16 +2 to +6V HC +5V LS/HCT
output Q1 2	0	15 input A (1)
output Q2 3		14 input B (2)
output Q3 4	7440	13 input C (4)
output Q4 5	7442	12 input D (8)
output Q5 6		11 output Q9
output Q6 7		10 output Q8
0V 8		9 output Q7